

Cory Snooks
Aaron Pederson
EE 465 Lab 1
9/9/2015

Verilog Coding and Test Bench for Simple Functions

Introduction

The purpose of this lab was to simulate a circuit using Verilog in Multisim. The desired outputs are shown in Figure 1 and the schematic view is shown in Figure 3. To get the proper delays, three output registers were used. The output was saved into oRESULTA or oRESULTB for one clock cycle before being added or assigned to oRESULT. The timescale was set to 10 ns to simulate a 50 MHz clock.

$$\text{oRESULT} = iA0 * iB0 + iA1 * iB1 + iA0 * iA1 * iB0 * iB1 \text{ when } iSEL = 0$$
$$\text{oRESULT} = iA0 * iB0 + iA1 * iB1 \text{ when } iSEL = 1$$

Figure 1: The required outputs are shown above for different values of iSEL.

- iCLK — input clock signal, 50MHz
- iRST_N — input reset signal, active Low
- iA0, iB0, iA1, iB1 — 8-bit binary unsigned integer input signals
- iSEL — input selection signal
- oRESULT — 17-bit binary unsigned integer output signal

Figure 2: The variable parameters used in this lab are shown above.

 


Figure 3: The schematic view of the required output is shown above.

Module Code

```
module test(iCLK, iRST_N, iSEL, iA0, iA1, iB0, iB1, oRESULT);
input iCLK, iRST_N, iSEL, iA0, iA1, iB0, iB1;
output oRESULT;

wire iCLK, iRST_N;
wire [7:0] iA0, iA1, iB0, iB1;
reg [16:0] oRESULTA, oRESULTB, oRESULT;

always @ (posedge iCLK)begin
  if(iRST_N)begin
    oRESULTA <= iA0 * iB0 + iA1 * iB1;
    oRESULTB <= iA0 * iB0 + iA1 * iB1 + iA0 * iA1 * iB0 * iB1;
    if(iSEL)begin
      oRESULT <= oRESULTA ;
    end
  else begin
    oRESULT <= oRESULTB;
  end
end
else begin
  oRESULT <= 0;
end
end

endmodule
```

Testbench

```
`timescale 10ns/1ns
module test_tb ();

reg iCLK_t, iRST_N_t, iSEL_t;
reg [7:0] iA0_t, iA1_t, iB0_t, iB1_t;
wire [16:0] oRESULT_t;

test X(iCLK_t, iRST_N_t, iSEL_t, iA0_t, iA1_t, iB0_t, iB1_t, oRESULT_t);

initial $display ("Test control");
  initial $display ("%10s %10s %10s %10s %10s %10s %10s %10s",
    "iCLK_t", "iRST_N_t", "iSEL_t", "iA0_t", "iA1_t",
    "iB0_t", "iB1_t", "oRESULT_t");
initial $monitor ("%10b %10b %10b %10d %10d %10d %10d %10d",
  iCLK_t, iRST_N_t, iSEL_t, iA0_t, iA1_t, iB0_t, iB1_t, oRESULT_t);
```

initial begin

```
iCLK_t = 0;  
iRST_N_t = 0;  
iSEL_t = 0;  
iA0_t = 0;  
iA1_t = 0;  
iB0_t = 0;  
iB1_t = 0;
```

```
#1  
iRST_N_t = 1;
```

```
#3  
iSEL_t = 1;  
iA0_t = 2;  
iA1_t = 3;  
iB0_t = 5;  
iB1_t = 1;
```

```
#10  
iSEL_t = 0;  
iA0_t = 2;  
iA1_t = 3;  
iB0_t = 5;  
iB1_t = 1;
```

```
#10  
iSEL_t = 1;  
iA0_t = 2;  
iA1_t = 3;  
iB0_t = 5;  
iB1_t = 1;
```

```
#10  
iSEL_t = 0;  
iA0_t = 53;  
iA1_t = 26;  
iB0_t = 120;  
iB1_t = 5;
```

```
#10  
iSEL_t = 0;  
iA0_t = 26;  
iA1_t = 1;  
iB0_t = 15;  
iB1_t = 19;
```

```
#4
$stop;
end
```

```
always #1 iCLK_t = ~iCLK_t;
endmodule
```

Figure 4 shows that the output was delayed two clock cycles after a change was recorded for the inputs. The first result is $iA0 * iB0 + iA1 * iB1 = 2 * 5 + 3 * 1 = 13$ because *iSEL* is high. The second result is after *iSEL* goes low and is $iA0 * iB0 + iA1 * iB1 + iA0 * iA1 * iB0 * iB1 = 13 + 2 * 3 * 5 * 1 = 43$.

 


Figure 4: The wave view from the test bench output is shown above.

Output

#	Test control							
#	iCLK_t	iRST_N_t	iSEL_t	iA0_t	iA1_t	iB0_t	iB1_t	oRESULT_t
#	0	0	0	0	0	0	0	x
#	1	1	0	0	0	0	0	x
#	0	1	0	0	0	0	0	x
#	1	1	0	0	0	0	0	0
#	0	1	1	2	3	5	1	0
#	1	1	1	2	3	5	1	0
#	0	1	1	2	3	5	1	0
#	1	1	1	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	0	2	3	5	1	13
#	1	1	0	2	3	5	1	43
#	0	1	0	2	3	5	1	43
#	1	1	0	2	3	5	1	43
#	0	1	0	2	3	5	1	43
#	1	1	0	2	3	5	1	43
#	0	1	0	2	3	5	1	43
#	1	1	0	2	3	5	1	43
#	0	1	0	2	3	5	1	43
#	1	1	0	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	1	2	3	5	1	13
#	1	1	1	2	3	5	1	13
#	0	1	0	53	26	120	5	13
#	1	1	0	53	26	120	5	43
#	0	1	0	53	26	120	5	43
#	1	1	0	53	26	120	5	46858
#	0	1	0	53	26	120	5	46858
#	1	1	0	53	26	120	5	46858

Figure 5: The output values are shown above.

Conclusion

This lab demonstrated how easy it is to go from concept to testing using Verilog. The only tricky part was getting the output to change with the correct delays to match the actual circuit output.