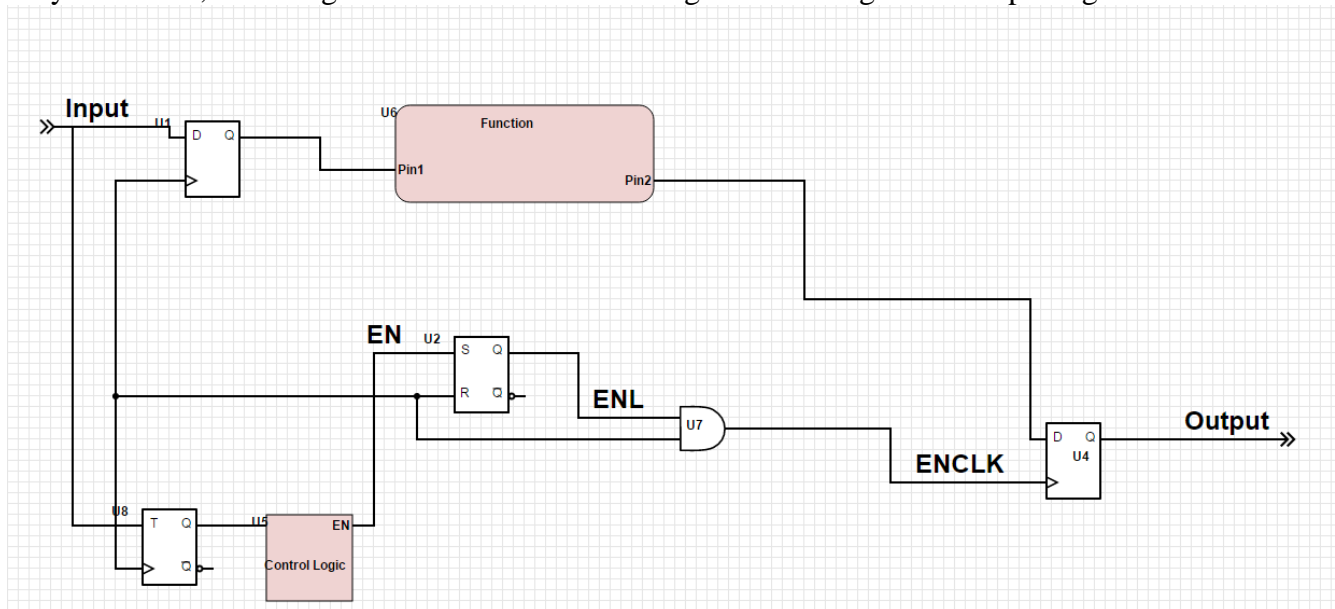


Lab 9 Report


The task of this lab is to reduce the power consumption of the circuit. In order to do this, we will eliminate any unnecessary switching of registers or gates. There are many possible registers that may be clock gated, but we will only do this for the output registers for time purposes.

1 DFF-based output clock gating


As you can see, this design uses a latch and an AND gate to clock-gate the output registers.




It will produce an output like this..

 

 
But if glitches are present in the control logic signal, there will be major problems as shown below with multiple clock edges at the output:



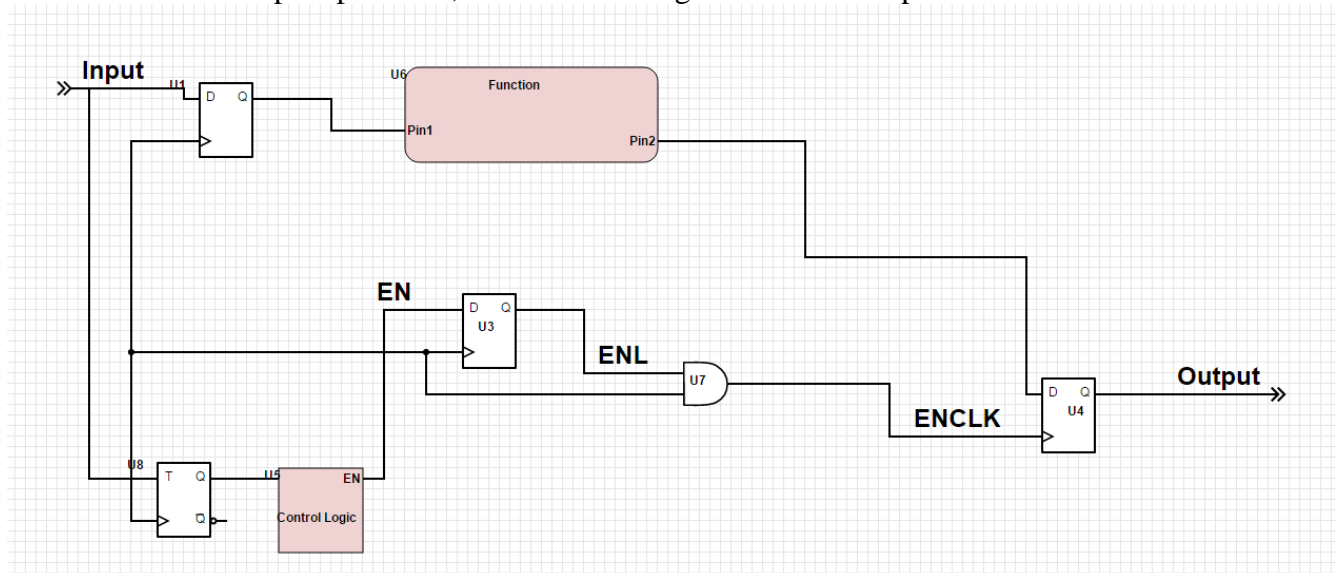So.. If we use a D-flip-flop instead, there will be no glitches at the output.



 
You can see that as long as the enable signal is high at the positive clock edge, the circuit will function properly.



2/3 Power-Efficient Design changes.

Before Change:

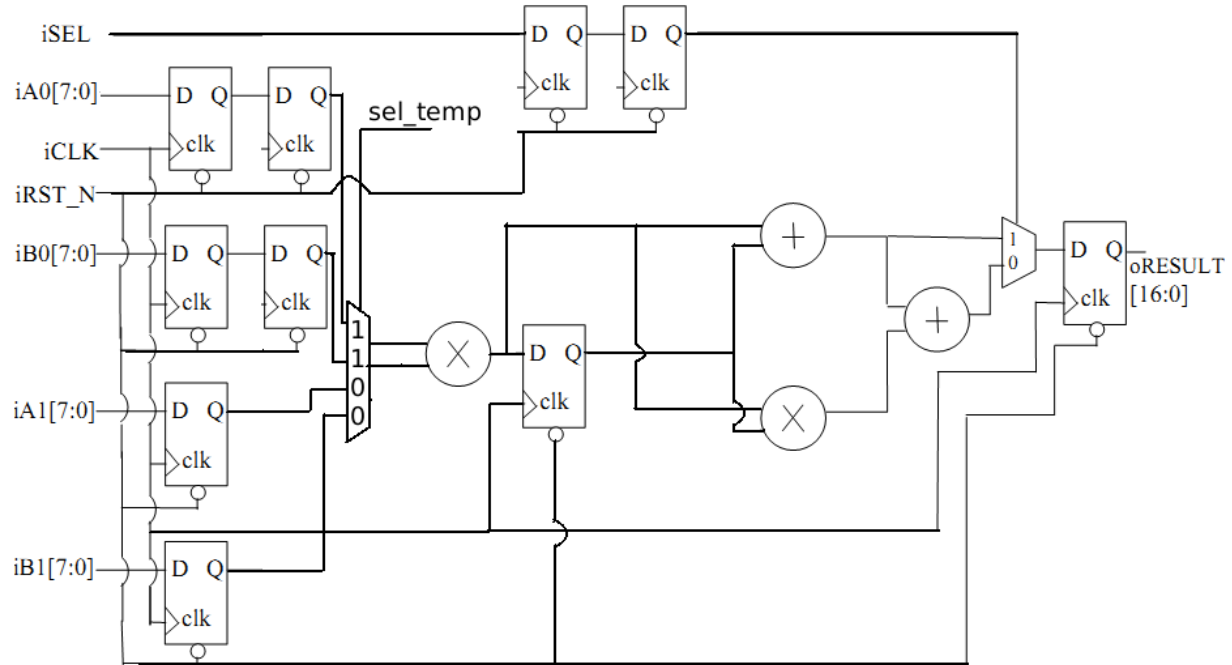The schematic diagram for the circuit before our changes for power efficiency is below:



```
module ALT_MULTADD_re(iCLK, iRST_N, iSEL, iSEL2, iA0, iA1, iB0, iB1, oR);
input iCLK, iRST_N, iSEL, iSEL2, iA0, iA1, iB0, iB1;
output oR;

wire iCLK, iRST_N, iSEL, iSEL2;
wire [7:0] iA0, iA1, iB0, iB1;
reg SEL1, SEL2, sel_tmp;
reg [7:0] A0, A1, B0, B1, A01, B01, AxB;
reg [16:0] oR;

always @ (posedge iCLK or negedge iRST_N)begin
A0 <= iA0;
B0 <= iB0;

A1 <= iA1;
B1 <= iB1;
A01 <= A0;
B01 <= B0;
SEL1 <= iSEL;
SEL2 <= SEL1;
sel_tmp <= iSEL2;

if(iRST_N)begin
if(~sel_tmp)begin
AxB <= A01 * B01;
end
else begin
AxB <= A1 * B1;
end
end
```

```

end

if(SEL2) begin
    oR <= AxB + A1 * B1;
end
else begin
    oR <= AxB + A1 * B1 + AxB * A1 * B1;
end
end
else begin
    sel_tmp <= 0;
    oR <= 0;
end
end

endmodule

```


With this version of my code, there is no control logic, so the iSEL_TMP signal serves as the indicator that a new input is present and must be a one clock cycle pulse. I intend to create control logic to create this signal automatically depending on the input signal edges.

After Change:

I decided to re-write the Verilog code to make it easier for the compiler to know to exactly construct the circuit.

I decided to re-introduce the internal control logic that would be triggered by edges on any of the input signals iA0,iA1,iB0,iB1 and iSEL. This would make the control logic for the enable signal for the clock gate much easier.

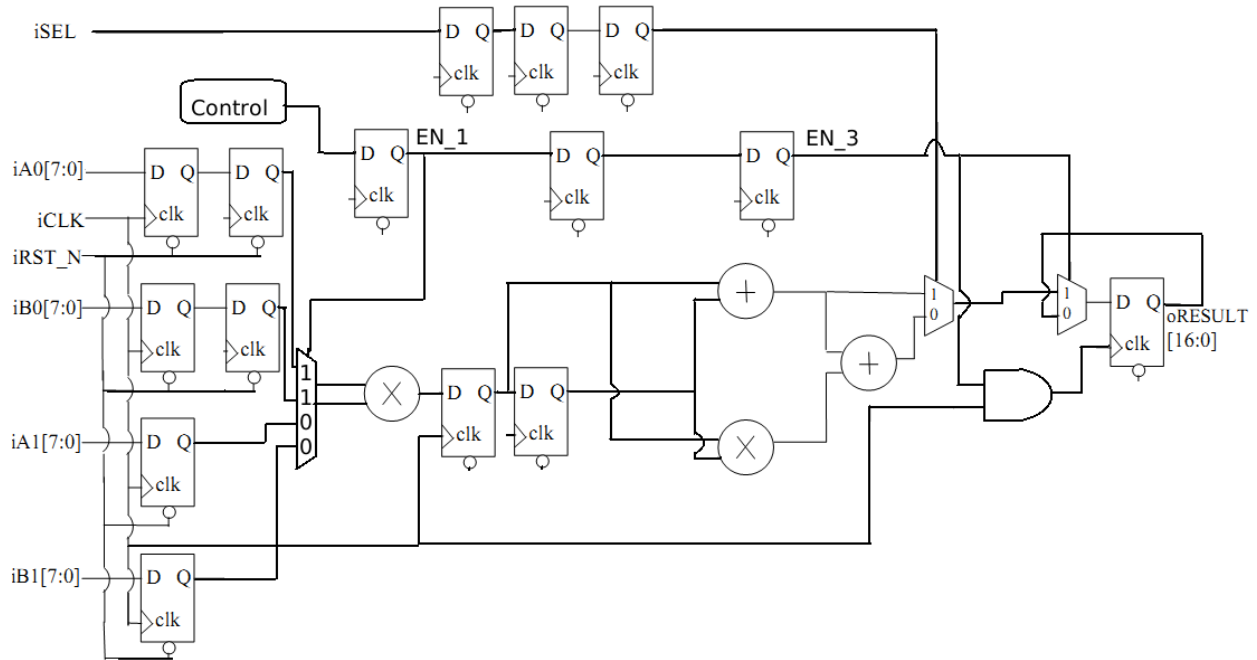I also added the optional d-flip flop after the first multiplier to fully pipeline the circuit.



As you can see, I changed the clock frequency to 5MHz by setting the timescale to 100ns which is half the clock cycle. $1s/200ns = 5MHz$.

```
`timescale 100ns/1ns
module ALT_MULTADD_9(iCLK, iRST_N, iSEL, iA0, iA1, iB0, iB1, oRESULT);
input iCLK, iRST_N, iSEL, iA0, iA1, iB0, iB1;
output oRESULT;

wire iCLK, iRST_N, iSEL;
wire [7:0] iA0, iA1, iB0, iB1;
reg SEL1, SEL2, SEL3, EN, EN_1, EN_2, EN_3;
reg [7:0] A0, A1, B0, B1, A01, B01, A, B;
reg [16:0] oR, AB, oRESULT, AB1_FF, AB0_FF;
reg go, no, no_FF, go_FF;

always @ (posedge iCLK)begin
if(~iRST_N)begin

A0 <= 0;
B0 <= 0;
A1 <= 0;
B1 <= 0;
A01 <= 0;
B01 <= 0;
```

```

SEL1 <= 0;
SEL2 <= 0;
SEL3 <= 0;

EN = 0;
EN_1 <= 0;
EN_2 <= 0;
EN_3 <= 0;

AB = 0;
AB1_FF <= 0;
AB0_FF <= 0;

go_FF <= 0;
no_FF <= 0;
go = 0;
no = 0;

oR = 0;
oRESULT <= 0;
end
else begin
    //Input registers
    A0 <= iA0;
    B0 <= iB0;
    A1 <= iA1;
    B1 <= iB1;
    A01 <= A0;
    B01 <= B0;

    //Multiplied signal registers
    AB1_FF <= AB;
    AB0_FF <= AB1_FF;

    //Select signal registers
    SEL1 <= iSEL;
    SEL2 <= SEL1;
    SEL3 <= SEL2;

    //enable(multiplexer select) signal registers
    EN_1 <= EN;
    EN_2 <= EN_1;
    EN_3 <= EN_2;

    //control logic stuff
    go_FF <= go;
    no_FF <= no;

    if(EN_3) begin
        oRESULT <= oR; //clock gate
    end
    //output register

end
end

//Select Control Logic
always@ (go_FF or EN_1 or no_FF) begin //
```

```

    if(go_FF ^ no_FF) begin //whenever no_FF and go_FF are different, that means
there is a new input.
        EN = 1;
        no = ~no_FF;
    end
    if(EN_1)begin
        EN = 0;
    end
end

// part of control logic
always @ (iA0 or iB0 or iA1 or iB1 or iSEL) begin
    go = ~go_FF;
end

//first stage of logic (multiplier)
always@ (EN_2 or A01 or B01 or A1 or B1) begin //
    if(EN_2)begin // this is the "multiplexer" for the multiplier
        A = A01;
        B = B01;
    end
    else begin
        A = A1;
        B = B1;
    end
    AB = A * B;
end

// final stage of logic
always@ (A01 or B01 or A1 or B1 or AB1_FF or AB0_FF) begin //
    if(SEL3) begin // this is the "multiplexer" 1 input of interest.
        oR = AB0_FF + AB1_FF;
    end
    else begin // this is the "multiplexer" 0 input of interest.
        oR = AB0_FF + AB1_FF + AB0_FF * AB1_FF;
    end
end
endmodule

```

We implemented the control logic with an always block triggered by changes in the inputs. We made 3 one bit registers go, no and count. When go and no are different, which will happen when the input changes because of the always block that inverts go, count will be set to 1 as well as no being inverted as well.

4 Verify

We made this test bench which would test the throughput of the circuit and many different inputs: After the initial input, we delayed the next input by #4 which means 2 clock cycles. We were able to get correct outputs with this so this means the expected maximum throughput is verified.

```
`timescale 100ns/1ns
module ALT_MULTADD_TB ();

    reg iCLK_t, iRST_N_t, iSEL_t;
    reg [7:0] iA0_t, iA1_t, iB0_t, iB1_t;
    wire [16:0] oRESULT_t;

    ALT_MULTADD_9 X(iCLK_t, iRST_N_t, iSEL_t, iA0_t, iA1_t, iB0_t, iB1_t, oRESULT_t);
    initial $display ("Test control");
    initial $display ("%10s %10s %10s %10s %10s %10s %10s %10s",
        "iCLK_t", "iRST_N_t", "iSEL_t", "iA0_t", "iA1_t",
        "iB0_t", "iB1_t", "oRESULT_t");
    initial $monitor ("%10b %10b %10b %10d %10d %10d %10d %10d",
        iCLK_t, iRST_N_t, iSEL_t, iA0_t, iA1_t, iB0_t, iB1_t, oRESULT_t);

    initial begin

        iCLK_t = 0;
        iRST_N_t = 0;
        iSEL_t = 0;
        iA0_t = 0;
        iA1_t = 0;
        iB0_t = 0;
        iB1_t = 0;

        #7
        iRST_N_t = 1;
        #1
        iA0_t = 3;
        iA1_t = 2;
        iB0_t = 3;
        iB1_t = 2;

        #4
        iSEL_t = 1;
        iA0_t = 1;
        iA1_t = 1;
        iB0_t = 1;
        iB1_t = 1;

        #4
        iA0_t = 2;
        iA1_t = 2;
        iB0_t = 2;
        iB1_t = 2;

        #4
```



```
iSEL_t = 0;  
iA0_t = 2;  
iA1_t = 2;  
iB0_t = 2;  
iB1_t = 6;
```

```
#4  
iA0_t = 1;  
iA1_t = 1;  
iB0_t = 1;  
iB1_t = 1;
```

```
#4  
iSEL_t = 1;  
iA0_t = 2;  
iA1_t = 2;  
iB0_t = 3;  
iB1_t = 3;
```

```
#4  
iSEL_t = 0;  
iA0_t = 1;  
iA1_t = 1;  
iB0_t = 1;  
iB1_t = 1;
```

```
#4  
iA0_t = 26;  
iA1_t = 1;  
iB0_t = 15;  
iB1_t = 19;
```

```
#4  
iSEL_t = 1;  
iA0_t = 26;  
iA1_t = 1;  
iB0_t = 15;  
iB1_t = 19;
```

```
#4  
iSEL_t = 1;  
iA0_t = 1;  
iA1_t = 2;  
iB0_t = 3;  
iB1_t = 4;
```

```
#4  
iSEL_t = 0;  
iA0_t = 1;  
iA1_t = 2;  
iB0_t = 3;  
iB1_t = 4;
```

```
#4  
iSEL_t = 1;  
iA0_t = 4;  
iA1_t = 3;
```

```

iB0_t = 2;
iB1_t = 1;

```

```

#4
iSEL_t = 0;
iA0_t = 4;
iA1_t = 3;
iB0_t = 2;
iB1_t = 1;

```

```

#20
$stop;

```

```

end

```

```

always #1 iCLK_t = ~iCLK_t;

```

```


endmodule

```

#	Test control	iCLK_t	IRST_N_t	iSEL_t	iA0_t	iA1_t	iB0_t	iB1_t	oRESULT_t
#	0	0	0	0	0	0	0	0	x
#	1	0	0	0	0	0	0	0	0
#	0	0	0	0	0	0	0	0	0
#	1	0	0	0	0	0	0	0	0
#	0	0	0	0	0	0	0	0	0
#	1	0	0	0	0	0	0	0	0
#	0	0	0	0	0	0	0	0	0
#	1	0	0	0	0	0	0	0	0
#	0	1	0	0	3	2	3	2	0
#	1	1	0	3	2	3	2	2	0
#	0	1	0	3	2	3	2	2	0
#	1	1	0	3	2	3	2	2	0
#	0	1	1	1	1	1	1	1	0
#	1	1	1	1	1	1	1	1	0
#	0	1	1	1	1	1	1	1	0
#	1	1	1	1	1	1	1	1	0
#	0	1	1	1	2	2	2	2	0
#	1	1	1	1	2	2	2	2	49
#	0	1	1	1	2	2	2	2	49
#	1	1	1	1	2	2	2	2	49
#	0	1	0	2	2	2	2	6	49
#	1	1	0	2	2	2	2	6	2
#	0	1	0	2	2	2	2	6	2
#	1	1	0	2	2	2	2	6	2
#	0	1	0	1	1	1	1	1	2
#	1	1	0	1	1	1	1	1	8
#	0	1	0	1	1	1	1	1	8
#	1	1	0	1	1	1	1	1	8
#	0	1	1	2	2	3	3	3	8
#	1	1	1	2	2	3	3	3	64
#	0	1	1	2	2	3	3	3	64
#	1	1	1	2	2	3	3	3	64
#	0	1	0	1	1	1	1	1	64
#	1	1	0	1	1	1	1	1	3
#	0	1	0	1	1	1	1	1	3
#	1	1	0	1	1	1	1	1	3
#	0	1	0	1	1	1	1	1	3
#	1	1	0	26	1	15	19	3	3
#	0	1	0	26	1	15	19	12	12
#	1	1	0	26	1	15	19	12	12
#	0	1	1	26	1	15	19	12	12
#	1	1	1	26	1	15	19	3	3
#	0	1	1	26	1	15	19	3	3
#	1	1	1	26	1	15	19	3	3
#	0	1	1	1	2	3	4	3	3
#	1	1	1	1	2	3	4	7819	7819
#	0	1	1	1	2	3	4	7819	7819
#	1	1	1	1	2	3	4	7819	7819
#	0	1	0	1	2	3	4	7819	7819
#	1	1	0	1	2	3	4	409	409
#	0	1	0	1	2	3	4	409	409
#	1	1	0	1	2	3	4	409	409
#	0	1	1	4	3	2	1	409	409
#	1	1	1	4	3	2	1	11	11
#	0	1	1	4	3	2	1	11	11
#	1	1	1	4	3	2	1	11	11
#	0	1	0	4	3	2	1	11	11
#	1	1	0	4	3	2	1	35	35
#	0	1	0	4	3	2	1	35	35
#	1	1	0	4	3	2	1	35	35
#	0	1	0	4	3	2	1	35	35

#	1	1	0	4	3	2	1	11
#	0	1	0	4	3	2	1	11
#	1	1	0	4	3	2	1	11
#	0	1	0	4	3	2	1	11
#	1	1	0	4	3	2	1	35
#	0	1	0	4	3	2	1	35
#	1	1	0	4	3	2	1	35
#	0	1	0	4	3	2	1	35
#	1	1	0	4	3	2	1	35
#	0	1	0	4	3	2	1	35
#	1	1	0	4	3	2	1	35
#	0	1	0	4	3	2	1	35
#	1	1	0	4	3	2	1	35
#	0	1	0	4	3	2	1	35
#	1	1	0	4	3	2	1	35
#	0	1	0	4	3	2	1	35

ns to 6843 ns

 

5 Synthesis:

In order to synthesize the Verilog code, I used this script.

```
## This sets the name of the directory in which area/timing/power reports
## and synthesized (mapped) netlists are stored.
set OUTPUT_DIR ./run_dir
if { ![file exists ${OUTPUT_DIR}] } { sh mkdir ${OUTPUT_DIR} }

#### Step 1 ####
## This tells the compiler where to look for the libraries
set_attribute lib_search_path ../libdir

## This defines the libraries to use
set_attribute library {tcbn65gpluswc.lib}
##set_attribute library {tcbn65gplustc.lib}
##set_attribute library {tcbn90ghpbc_ccs.lib}
##set_attribute lp_insert_clock_gating true

#set attribute lp insert operand isolation true
#rm /designs/*

#### Step 2 ####
##This must point to your VHDL/verilog file
load -v2001 ../ALT_MULTADD_redid.v
set_attribute lp_insert_clock_gating false

#### Step 3 ####
## This builds the general block
elaborate


dc::set_time_unit -nanoseconds
dc::set_load_unit -picofarads
define_clock -period 200 -name clk [dc::get_ports {iCLK}] -rise 5 -fall 5
set_attribute lp_power_unit {nW}
set_attribute max_leakage_power 100000 /designs/ALT_MULTADD_9

set_attribute power_optimization_effort high
synthesize -to_mapped -effort high

report area > ${OUTPUT_DIR}/area.rpt
report gates > ${OUTPUT_DIR}/gates.rpt
report timing > ${OUTPUT_DIR}/timing.rpt
report timing -lint > ${OUTPUT_DIR}/lint.rpt
report summary > ${OUTPUT_DIR}/summary.rpt
report power > ${OUTPUT_DIR}/power.rpt

write -mapped > ${OUTPUT_DIR}/jpeg_mapped.v
write_script > ${OUTPUT_DIR}/jpeg_mapped.g
```

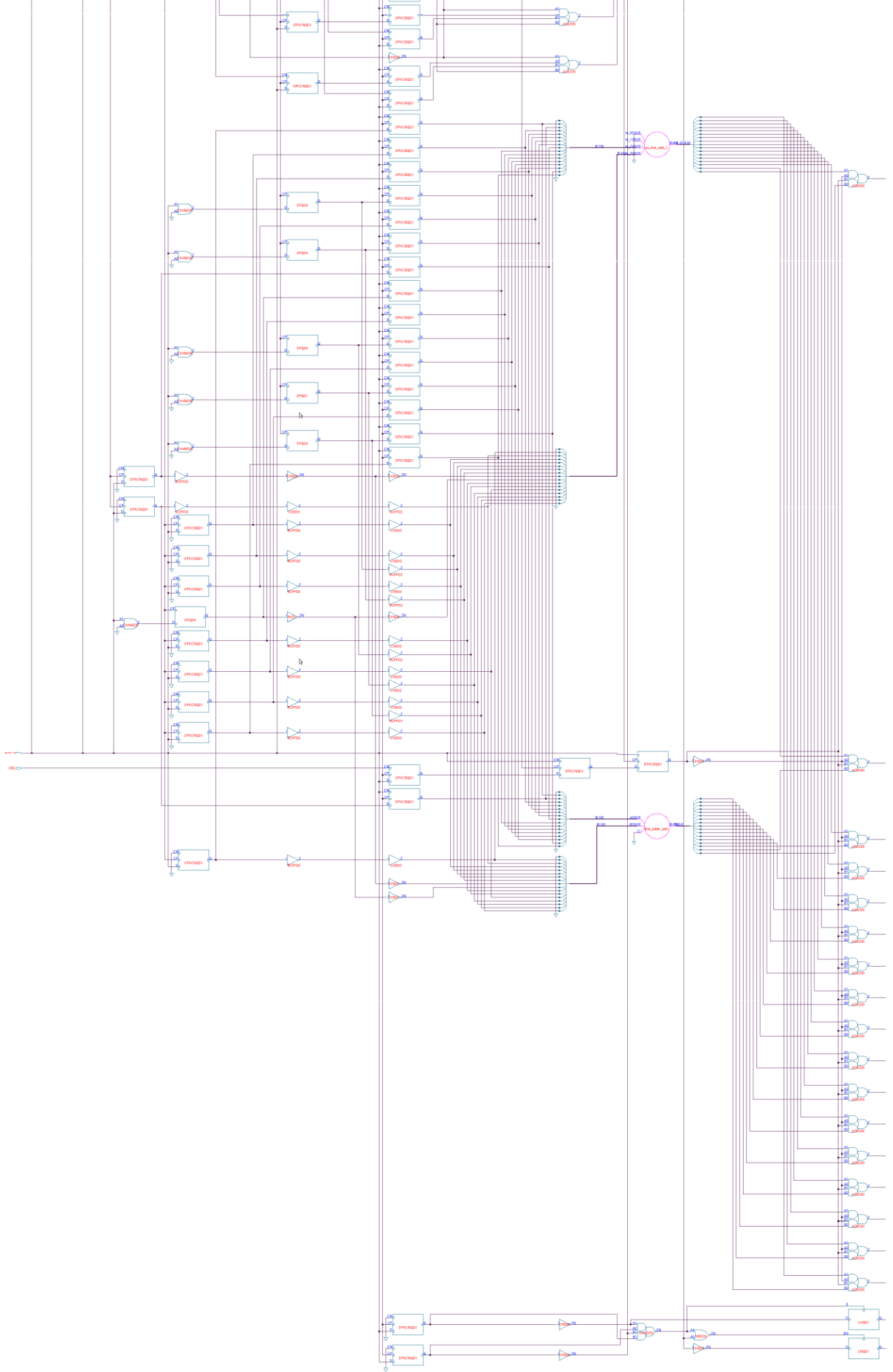The diagram illustrates a 16-bit adder circuit. It consists of a central column of 16 full adders (FA0 to FA15) and a carry chain on the right. The circuit includes multiple multiplexers (MUX), AND/OR gates, and a carry-in input. The final 16-bit sum is output as 'sum[15:0]'.



Power, Area and Timing reports:

Power:

Instance	Cells	Leakage Power (nW)	Dynamic Power (nW)	Total Power (nW)
ALT_MULTADD_9	788	25576.140	3670617.854	3696193.994
csa_tree_a..116_30_groupi	392	10639.582	0.000	10639.582
mul_106_12	135	5552.124	0.000	5552.124
final_adder_add_113_21	18	1633.508	0.000	1633.508

Area:

Instance	Cells	Cell Area	Net Area	Wireload
ALT_MULTADD_9	788	3167	0	ZeroWireload (S)
csa_tree_add_116_30_groupi	392	1377	0	ZeroWireload (S)
mul_106_12	135	590	0	ZeroWireload (S)
final_adder_add_113_21	18	144	0	ZeroWireload (S)

Timing:

Pin	Type	Fanout	Load (fF)	Slew (ps)	Delay (ps)	Arrival (ps)
(clock clk)	launch					10 R
EN_3_reg/CP				0		10 R
EN_3_reg/Q	DFKCNQD4	2	13.6	31	+123	133 F
g1946/A1					+0	133
g1946/ZN	NR2XD8	17	19.4	35	+29	162 R
g1669/A2					+0	162
g1669/ZN	CKND2D1	1	1.2	25	+28	190 F
g1668/A1					+0	190
g1668/ZN	ND2D1	1	1.1	21	+20	210 R
oRESULT_reg[9]/D	DFQD1				+0	210
oRESULT_reg[9]/CP	setup			0	+30	240 R
(clock clk)	capture					210 R

Timing slack : -30ps (TIMING VIOLATION)
Start-point : EN_3_reg/CP
End-point : oRESULT_reg[9]/D

Clock gating report:

With the command “report clock_gating -summary” I got the following report:

Summary

Category	Number	%
RC Clock Gating Instances	0	-
Non-RC Clock Gating Instances	0	-
RC Gated Flip-flops	0	0
Non-RC Gated Flip-flops	0	0
Ungated Flip-flops	105	100
Total Flip-flops	105	100

Obviously because I didn't enable clock gating there were no clocks gated.

Synthesis with clock gating enabled:

```
## This sets the name of the directory in which area/timing/power reports
## and synthesized (mapped) netlists are stored.
set OUTPUT_DIR ./run_dir
if { ![file exists ${OUTPUT_DIR}] } { sh mkdir ${OUTPUT_DIR} }

#### Step 1 ####
## This tells the compiler where to look for the libraries
set_attribute lib_search_path ../libdir

## This defines the libraries to use
set_attribute library {tcbn65gpluswc.lib}
##set_attribute library {tcbn65gplustc.lib}
##set_attribute library {tcbn90ghpbc_ccs.lib}
##set_attribute lp_insert_clock_gating true

#set_attribute lp_insert_operand_isolation true
#rm /designs/*

#### Step 2 ####
##This must point to your VHDL/verilog file
load -v2001 ../../ALT_MULTADD_redid.v

set_attribute lp_insert_clock_gating true

#### Step 3 ####
## This builds the general block
elaborate


dc::set_time_unit -nanoseconds
dc::set_load_unit -picofarads
define_clock -period 200 -name clk [dc::get_ports {iCLK}] -rise 5 -fall 5
set_attribute lp_power_unit {nW}
set_attribute max_leakage_power 100000 /designs/ALT_MULTADD_9

set_attribute power_optimization_effort high
synthesize -to_mapped -effort high


report area > ${OUTPUT_DIR}/area.rpt
report gates > ${OUTPUT_DIR}/gates.rpt
report timing > ${OUTPUT_DIR}/timing.rpt
report timing -lint > ${OUTPUT_DIR}/lint.rpt
report summary > ${OUTPUT_DIR}/summary.rpt
report power > ${OUTPUT_DIR}/power.rpt

write -mapped > ${OUTPUT_DIR}/jpeg_mapped.v
write_script > ${OUTPUT_DIR}/jpeg_mapped.g
write_sdc > ${OUTPUT_DIR}/jpeg_mapped.sdc
```

Clock gater

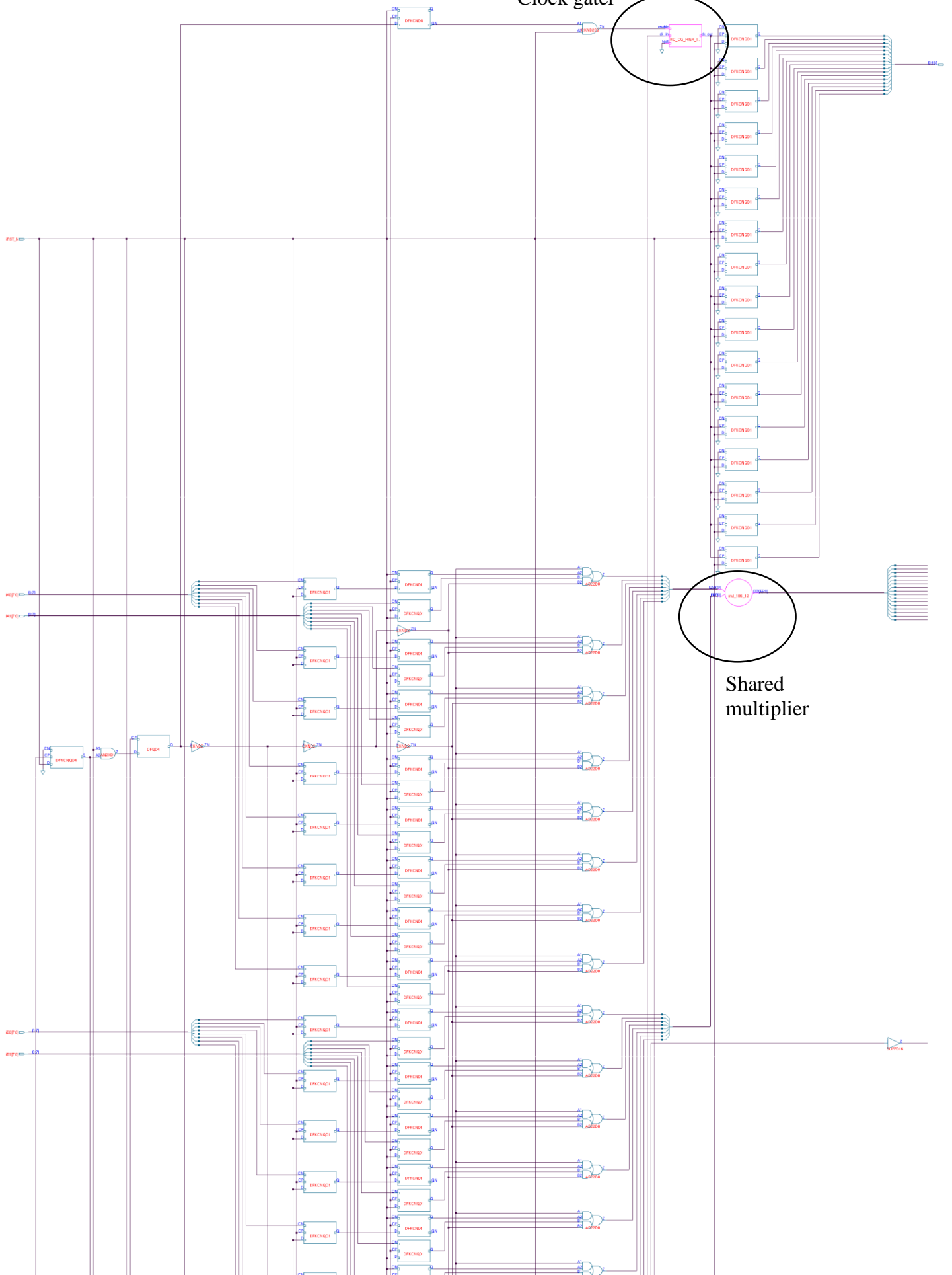

Shared
multiplier

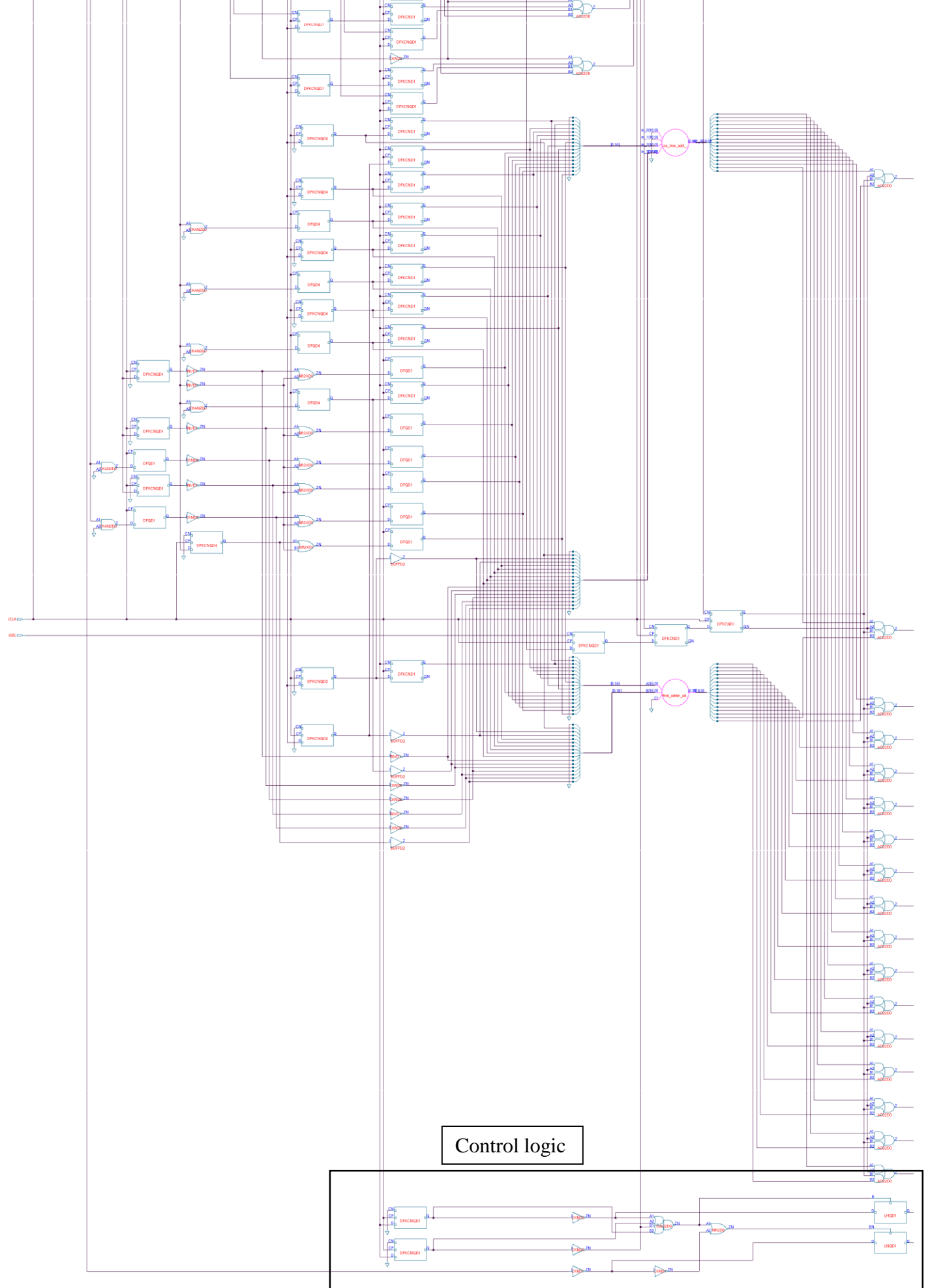

Power, Area and Timing reports:

Power:

Instance	Cells	Leakage Power (nW)	Dynamic Power (nW)	Total Power (nW)
ALT_MULTADD_9	714	24911.327	3187026.832	3211938.160
csa_tree_a..116_30_groupi	379	10296.895	0.000	10296.895
mul_106_12	135	5552.124	0.000	5552.124
final_adder_add_113_21	18	1633.508	0.000	1633.508
RC_CG_HIER_INST0	1	41.593	23555.208	23596.801

Dynamic and total power consumption decreased as expected due to the clock gating being enabled.

Area:

Instance	Cells	Cell Area	Net Area	Wireload
ALT_MULTADD_9	714	3080	0	ZeroWireload (S)
csa_tree_add_116_30_groupi	379	1356	0	ZeroWireload (S)
mul_106_12	135	590	0	ZeroWireload (S)
final_adder_add_113_21	18	144	0	ZeroWireload (S)
RC_CG_HIER_INST0	1	6	0	ZeroWireload (S)

Area decreased due to replacement of AOI gates with the clock gate.

Timing:

Pin	Type	Fanout	Load (fF)	Slew (ps)	Delay (ps)	Arrival (ps)
(clock clk)	launch					10 R
EN_3_reg/CP				0		10 R
EN_3_reg/QN	DFKCND4	1	1.9	16	+154	164 R
g1263/A1					+0	164
g1263/ZN	CKND2D2	1	1.0	14	+15	178 F
RC_CG_HIER_INST0/enable						
RC_CGIC_INST/E	CKLNQD1				+0	178
RC_CGIC_INST/CP	setup			0	+47	226 R
(clock clk)	capture					210 R

Cost Group : 'cg_enable_group_clk' (path_group 'cg_enable_group_clk')
Timing slack : -16ps (TIMING VIOLATION)
Start-point : EN_3_reg/CP
End-point : RC_CG_HIER_INST0/RC_CGIC_INST/E

Timing slack improved slightly.

Clock gating report:

With the command “report clock_gating -summary” I got the following report:

Summary

Category	Number	%

RC Clock Gating Instances	1	-
Non-RC Clock Gating Instances	0	-

RC Gated Flip-flops	17	16
Non-RC Gated Flip-flops	0	0
Ungated Flip-flops	88	84
Total Flip-flops	105	100

Conclusion

As we have mentioned before, the coding style dramatically effects the synthesized circuit. We can see this clearly now that we have changed the code to be more modular and to not set registers in multiple always blocks. There are improvements in all specifications of the circuit. As for the changes caused by the clock gating, it is hard to tell if it alone improved specifications because it may be only due to the changed coding style. I had a hard time getting the clock gating to synthesize correctly but finally found that I needed to put the if statement in the always block for the registers which I was clock gating.